



03


FRIDAY
MAY

2019

Assignment - 5

D Given $k_n C_{ox} = 100 \mu A/V^2$ $\frac{W}{L} = 1$ $V_T = 1V$ $I_0 = 200 \mu A$
 $\beta = k_n C_{ox} \frac{W}{L} = 100 \mu A/V^2$

(a)

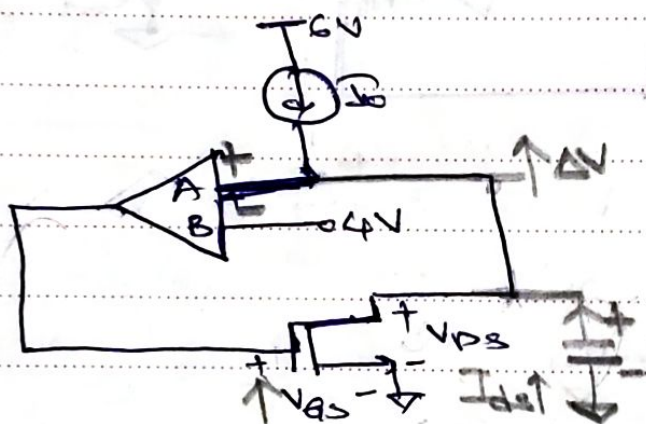

Sense: Drain

Control: Gate

Now let's assume $A(+)$ and $B(-)$. For finding right feedback, let's slightly increment the sensing voltage by ΔV at V_D . If the feedback is -ve, this V_D has to re-established.

When $V_D \rightarrow V_D + \Delta V$, $V_G \rightarrow V_G + A\Delta V$, when $V_G \uparrow$, $V_{GS} \uparrow$ and so does I_{DS} . Hence $I_{DS} > I_0$, this residual current has to be supplied by the parasitic capacitance, there by reducing its voltage, which makes $V_D \downarrow$. Hence, for given sign configuration, The feedback is -ve. i.e. $A(+ve)$; $B(-ve)$.

Then,

$$V_{DS} = 4V \text{ --- (Virtual short)}$$



04

SATURDAY
MAY


2019

And $I_{ds} = \frac{\beta}{2} (V_{gs} - V_T)^2$

$$\Rightarrow V_{gs} = V_T + \sqrt{\frac{2I_{ds}}{\beta}} = 1 + \sqrt{\frac{2 \times 200 \mu}{100 \mu}} = 3V$$

$$\therefore V_{gs} = 3V \text{ and } V_{ds} = 4V$$

Now for using it as common source amplifier, the output can be extracted from drain, as op amp has high input impedance, all current flows through the MOS. But for input, a series high resistance is needed to be connected with op amp to prevent input current flow through op amp, not offering high input impedance as shown.

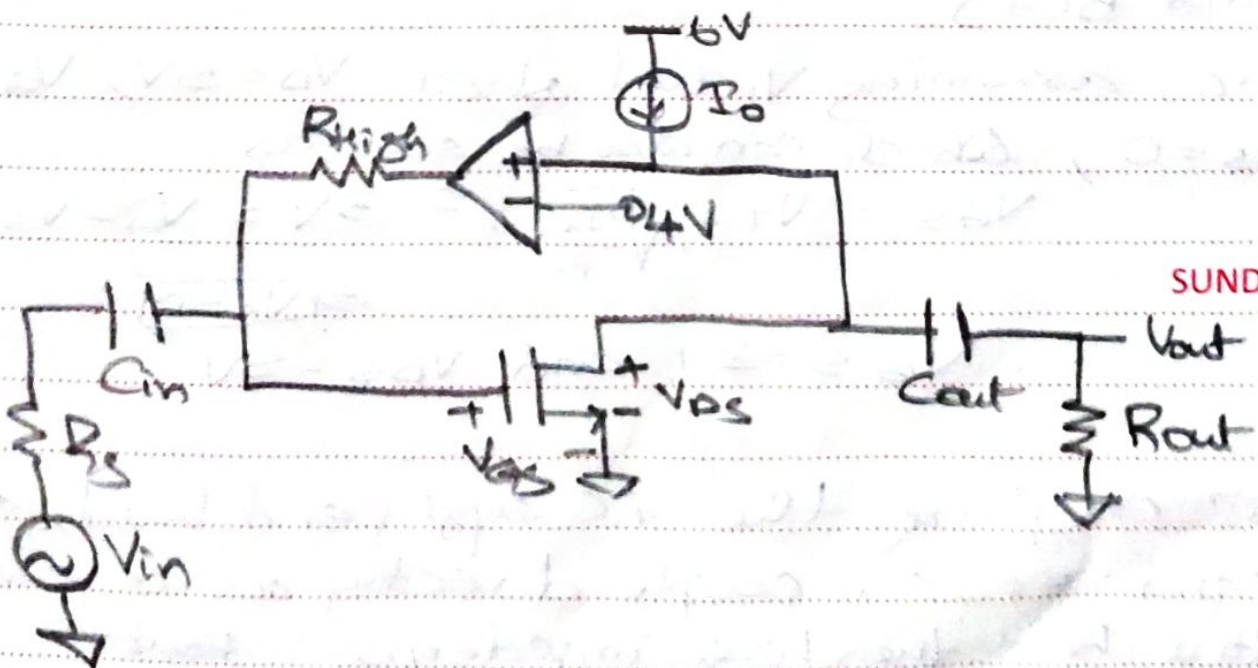

SUNDAY 05




16

THURSDAY
MAY

2019


Alter: Finding Feedback by cutting loop

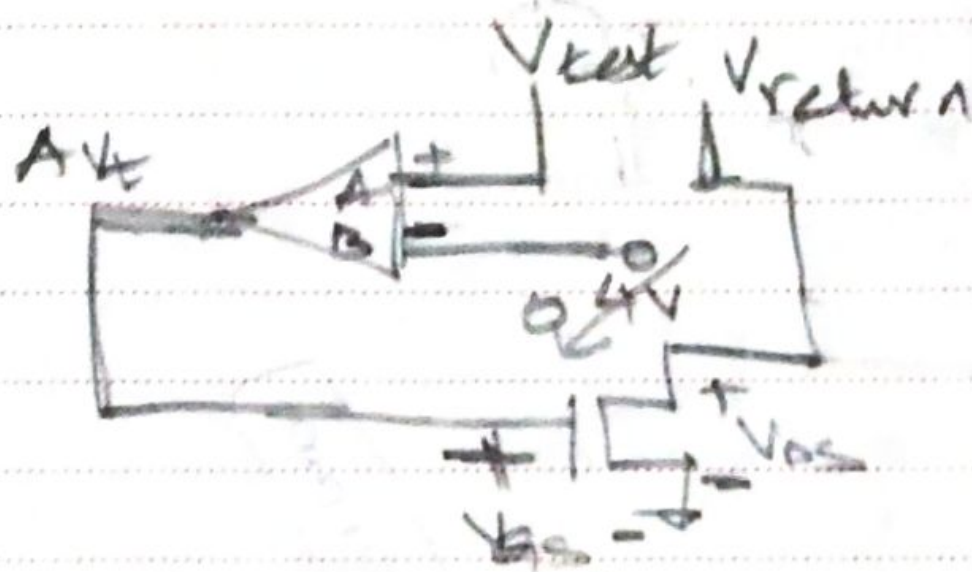

cut at input
of opamp

Here,

$$V_{return} = -R_{oD}$$

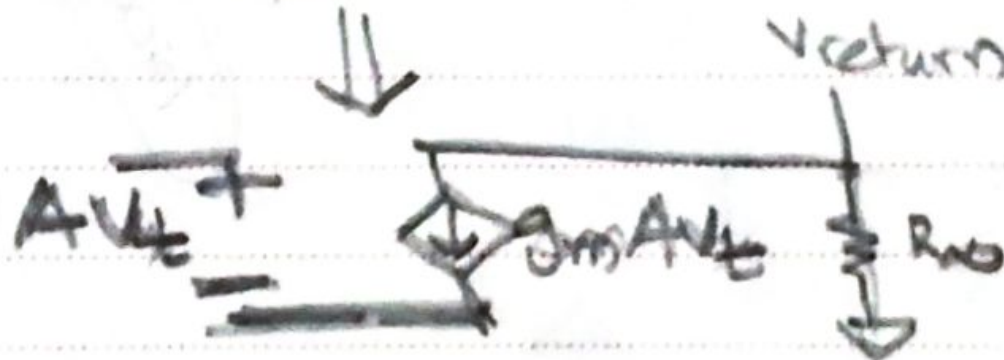

$$\begin{aligned} V_{return} &= -R_o \cdot g_m A_{vt} \\ &= -\infty \\ &= -ve \end{aligned}$$

∴ This sign

of A_{vt} gives $-ve$ to




06

MONDAY

MAY

2019

b)

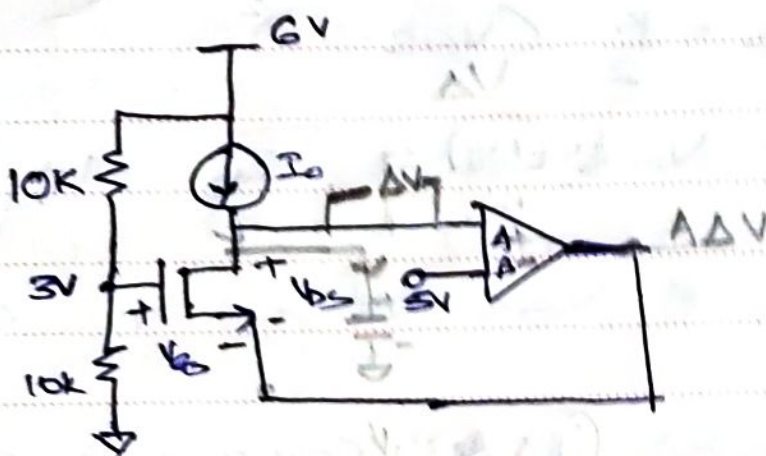Sense: Drain
Control: Source

Let assume $A(+)$ and $B(-)$. A small ΔV perturbed at V_D . Then V_S will increase by $A\Delta V$. When $V_S \uparrow$, $V_{GS} \downarrow$ and so does I_{DS} . Here $I_D > I_{DS}$, so the rest current flows through the cap. there by even increasing the V_D , hence is seeing as +ve feedback. For -ve feedback we have to switch the terminals i.e $A(-)$ and $B(+)$.

here, assuming virtual short $V_D = 5V$, $V_G = 3V$
 $V_S = 0$, which can also be seen as

$$V_{GS} = V_T + \sqrt{\frac{2I_{DS}}{\mu C_{ox} W/L}} = 3V = V_G - V_S$$

$\Rightarrow (V_S = 0)$

$$\therefore V_{GS} = 3V \text{ and } V_{DS} = 5V$$


For coupling the AC supply and load, at input we can couple directly as we can still have the high impedance. But




07

TUESDAY
MAY 2019

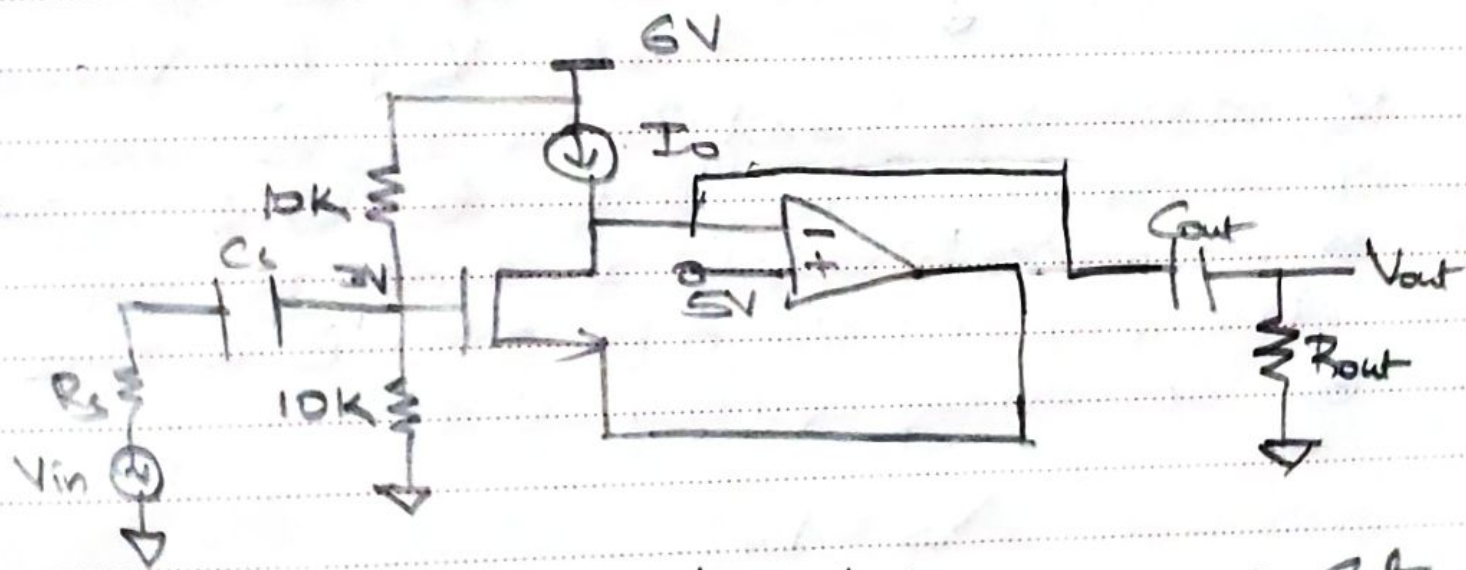output, the current from op-amp interferes with the output's current. To limit the current from op-amp, we can add a high resistance connected to output as shown.



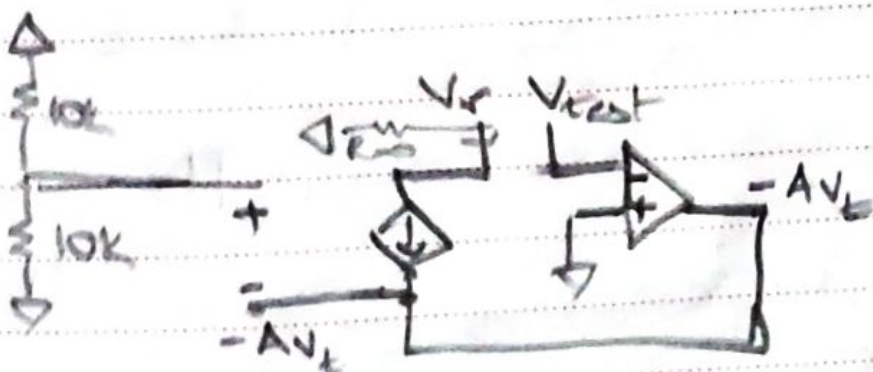Alter: For finding the f.b, we can cut loop at input of op-amp.



Hence,

$$V_r = -R_{out} \cdot A_{v_t}$$

$$= -\infty$$

$$= -ve$$

∴ Feedback is -ve

$$V_{in} = A_{v_t} V_{out}$$


$$\Rightarrow I_{in} = I_{out}$$



08

WEDNESDAY
MAY 2019

c)

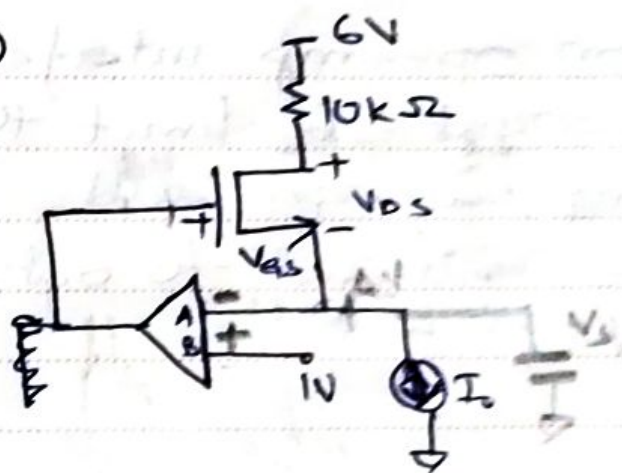

Sense: Source

Control: Gate

By giving a small delta increment at sensing voltage, we observe $V_{GS} \uparrow$, $V_{DS} \downarrow$ by $-A_{VS}$. Hence

V_{GS} decreases and hence I_{DS} decreases. To maintain I_D , the parasitic cap at source discharges, decreasing the increment. \therefore A is $-ve$, B is $+ve$.

By assuming virtual short,

$$V_S = 1V$$

$$V_{DS} = (6V - 10K \times 200\mu A) - 1V \\ = 3V$$

$$\text{And } V_{GS} = V_T + \sqrt{\frac{2I_{DS}}{\beta}} = 1 + 2 = 3V$$

$$\therefore V_{DS} = 3V \text{ and } V_{GS} = 3V$$

Here the input impedance is not high, as the op-amps output terminal can load the input and hence we connect high series resistance.




09

THURSDAY


MAY

2019

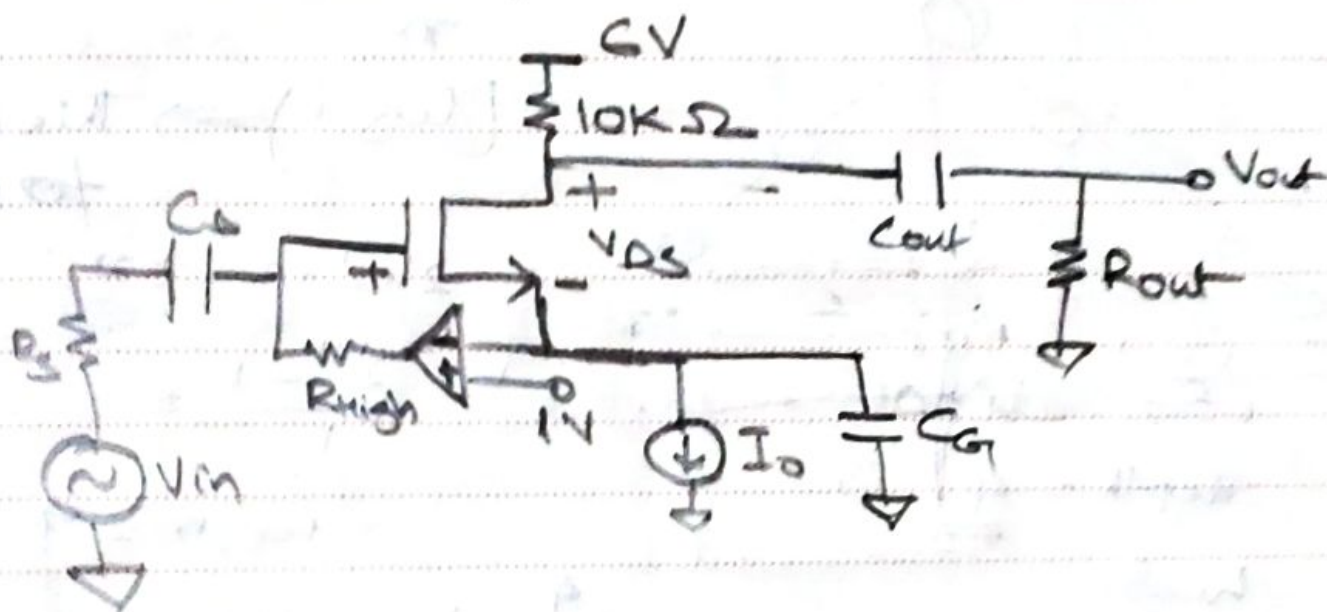The output is fine to connect as, the current is flowing completely between MOS and the output resistor.



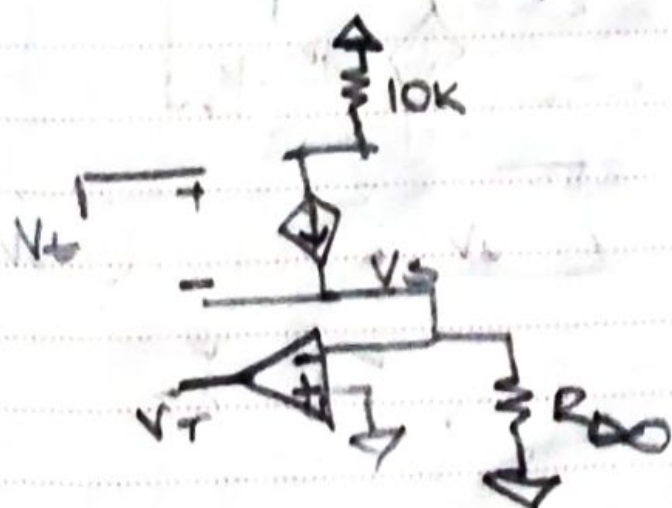Alter: For finding feed back, we can also cut the loop and apply test voltage. Suppose we cut it at input of MOS, we get



$$V_s = g_m (V_t - V_s) \cdot R_L$$

$$\Rightarrow V_s = g_m R_{th} (V_t - V_s)$$

$$V_s = \frac{g_m R_{th} V_t}{1 + g_m R_{th}} \approx V_t$$




$$\Rightarrow V_r = -V_t \cdot A < 0$$

$\Rightarrow -ve$ f.b for given sign.



Mo Tu We Th Fr Sa Su

Date / /

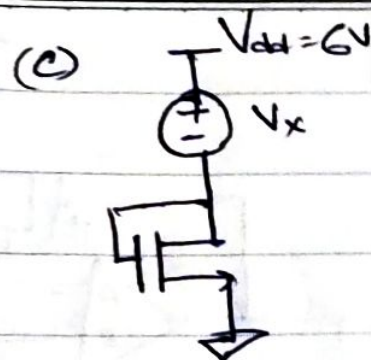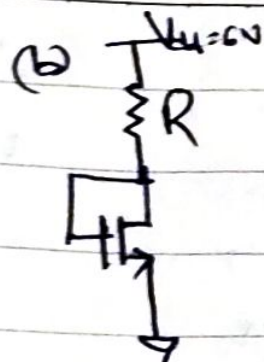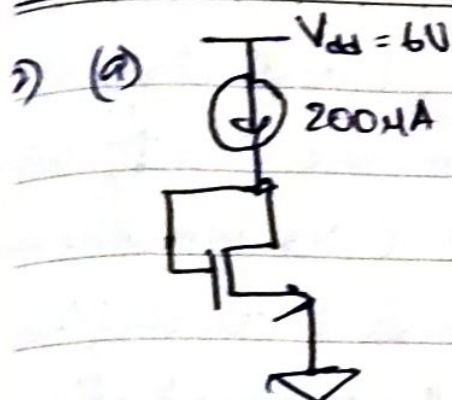


$$\mu_n C_{ox} = 100 \mu A/V^2 \quad \frac{W}{L} = 1 \quad V_T = 1V$$
$$B = 100 \mu A/V^2$$

For (a) Operating point is

$$V_{GS} = V_T + \sqrt{\frac{2I_{DQ}}{B}} = 1 + \sqrt{\frac{2 \times 200 \mu A}{100 \mu A/V^2}} = 3V$$
$$\Rightarrow \boxed{V_{GS} = 3V}$$

And Gate/drain are shorted $\Rightarrow \boxed{V_{GS} = V_{DS} = 3V}$

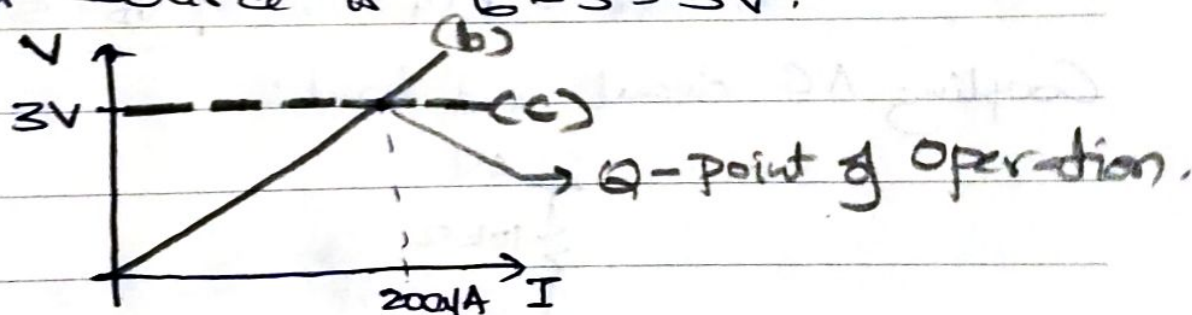As $V_S = 0 \Rightarrow V_D = 3V$. Voltage drop across the current source is $6 - 3 = 3V$.



For the given point of operation, in (b), R should be such that it has same voltage drop across i.e 3V and has to pass same current i.e 200 μA. Then

$$R = \frac{V}{I} = \frac{3V}{200 \times 10^{-6} A} = 1.5 \times 10^4 \Omega = 15K\Omega$$

$$\Rightarrow \boxed{R = 15K\Omega}$$



Similarly, for (c) the drop across the battery has to be 3V and should maintain 200 μA . As a voltage source remains same for all currents we can take,

$$V_x = 3V$$

(ii) Supply change: ΔV_{DD} is given.

Case - a: The I_{DS} is driven by current source and change in supply voltage is taken care by the current source.

$$\Rightarrow \Delta I_{DS} = 0$$

$$\text{Case - b: Here } I_{DS} = \frac{\beta}{2} (V_{GS} - V_T)^2 \\ = \frac{\beta}{2} (V_{DD} - I_{DS}R - V_T)^2$$

$$\Rightarrow \frac{\partial I_{DS}}{\partial V_{DD}} = \beta (V_{DD} - I_{DS}R - V_T) \cdot \left(\frac{\partial V_{DD}}{\partial V_{DD}} - R \frac{\partial I_{DS}}{\partial V_{DD}} \right)$$

$$= 100 \times 10^6 \times 2 \left(1 - 15 \times 10^3 \frac{\partial I_{DS}}{\partial V_{DD}} \right)$$

$$\Rightarrow \frac{\partial I_{DS}}{\partial V_{DD}} = \frac{2 \times 100 \times 10^6}{1 + 100 \times 10^6 \times 2 \times 15 \times 10^3} = 50 \times 10^{-6}$$

$$\Rightarrow \Delta I_{DS} = \left. \frac{\partial I_{DS}}{\partial V_{DD}} \right|_{V_{DS}=3V} \cdot \Delta V_{DD} = \boxed{50 \times 10^{-6} \Delta V_{DD}}$$

Case - c: Here $V_{GS} = V_{DS} = V_{DD} - V_x$; $I_{DS} = \frac{\beta}{2} (V_{GS} - V_T)^2$

$$\Rightarrow \frac{\partial I_{DS}}{\partial V_{DD}} = \beta (V_{GS} - V_T) \left[\frac{\partial V_{GS}}{\partial V_{DD}} \right] = 100 \times 10^6 \times 2 \times \frac{\partial (V_{DD} - V_x)}{\partial V_{DD}}$$

$$= 200 \times 10^6 \times 1 \\ \Rightarrow \boxed{\Delta I_{DS} = 200 \times 10^6 \times \Delta V_{DD}}$$



iii) Effect of change in V_T .

Case-a: The current I_{DS} is driven by external current source and change V_T results in change in V_{GS} and V_{DS} but I_{DS} remains same.

$$\begin{aligned}\text{Case-b: } I_{DS} &= \frac{\beta}{2} (V_{GS} - V_T)^2 \\ &= \frac{\beta}{2} (V_{DD} - I_{DS} R_S - V_T)^2\end{aligned}$$

$$\begin{aligned}\Rightarrow \frac{\partial I_{DS}}{\partial V_T} &= \beta (V_{DD} - I_{DS} R_S - V_T) (-1) \\ &= 100 \times 10^{-6} (2) (-1) = -200 \times 10^{-6}\end{aligned}$$


$$\Rightarrow \Delta I_{DS} = -200 \times 10^{-6} \times \Delta V_T$$

$$\text{Case-c: } I_{DS} = \frac{\beta}{2} (V_{GS} - V_T)^2 = \frac{\beta}{2} (V_{DD} - V_X - V_T)^2$$

$$\Rightarrow \frac{\partial I_{DS}}{\partial V_T} = \beta (V_{DD} - V_X - V_T) \cdot \frac{\partial V_T}{\partial V_T} = -\beta (V_{DD} - V_X - V_T)$$

$$= -100 \times 10^{-6} \times (2) = -200 \times 10^{-6}$$
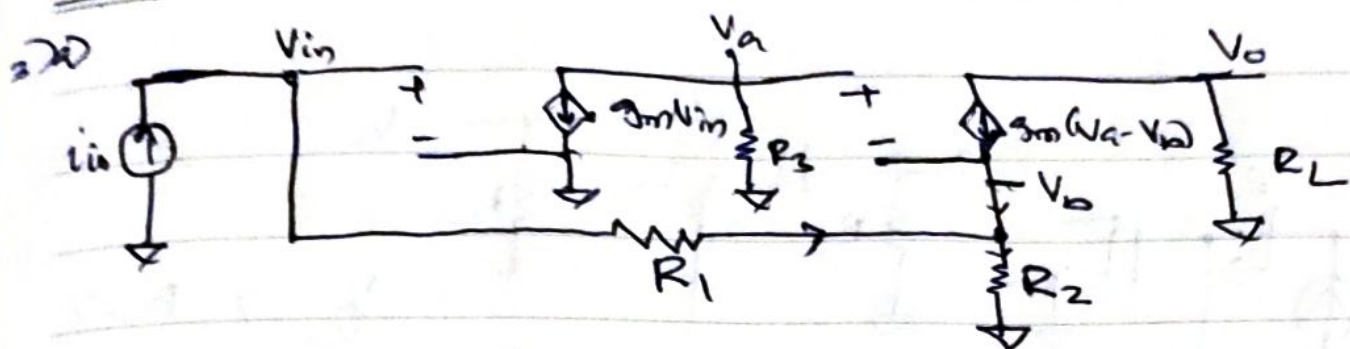
$$\Rightarrow \Delta I_{DS} = -200 \times 10^{-6} \Delta V_T$$



$$V_a = -g_m V_{in} R_3 \quad V_o = -g_m R_L (V_a - V_b)$$

$$\Rightarrow \frac{V_{in} - V_b}{R_1} + g_m (V_a - V_b) = \frac{V_b}{R_2}$$

$$\Rightarrow \frac{V_{in} - V_b}{R_1} + g_m (-g_m V_{in} R_3 - V_b) = \frac{V_b}{R_2}$$

$$\Rightarrow V_{in} \left(\frac{1}{R_1} - g_m^2 R_3 \right) = V_b \left[\frac{1}{R_1} + \frac{1}{R_2} + g_m \right]$$

$$\Rightarrow V_b = V_{in} \frac{\left(\frac{1}{R_1} - g_m^2 R_3 \right)}{\left(\frac{1}{R_1} + \frac{1}{R_2} + g_m \right)}$$

$$i_{in} = \frac{V_{in} - V_b}{R_1} = \frac{V_{in}}{R_1} \left[1 - \frac{\left(\frac{1}{R_1} - g_m^2 R_3 \right)}{\left(\frac{1}{R_1} + \frac{1}{R_2} + g_m \right)} \right]$$

$$= \frac{V_{in}}{R_1} \left[\frac{\frac{1}{R_2} + g_m + g_m^2 R_3}{\frac{1}{R_1} + \frac{1}{R_2} + g_m} \right]$$

$$= V_{in} \left[\frac{1 + g_m R_2 + g_m^2 R_3 R_2}{R_1 + R_2 + g_m R_1 R_2} \right]$$

$$\Rightarrow R_{in} = \frac{V_{in}}{i_{in}} = \frac{R_1 + R_2 + g_m R_1 R_2}{1 + g_m R_2 + g_m^2 R_3 R_2}$$



Mo Tu We Th Fr Sa Su

Date / /

$$\text{Now, } V_o = -g_m R_L (V_a - V_b)$$

$$\Rightarrow V_o = -g_m R_L \left(-g_m V_{in} R_3 - V_{in} \left(\frac{1}{R_1} - g_m^2 R_3 \right) \right)$$

$$= g_m R_L V_{in} \left[g_m R_3 + \left(\frac{1}{R_1} - g_m^2 R_3 \right) \right]$$

$$= g_m R_L V_{in} \left[\frac{g_m^2 R_3 + g_m R_3 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{1}{R_1} - g_m^2 R_3}{\frac{1}{R_1} + \frac{1}{R_2} + g_m} \right]$$

$$= g_m R_L V_{in} \left[\frac{g_m R_3 (R_1 + R_2) + R_2}{R_1 + R_2 + g_m R_1 R_2} \right]$$

$$= g_m R_L \cdot i_{in} R_{in} \left[\frac{g_m (R_3 (R_1 + R_2) + R_2)}{R_1 + R_2 + g_m R_1 R_2} \right]$$

$$\frac{V_o}{i_{in}} = g_m R_L \left[\frac{g_m (R_3 (R_1 + R_2) + R_2)}{1 + g_m R_2 + g_m^2 R_2 R_3} \right]$$

When $g_m \rightarrow \infty$,

$$R_{in} = \lim_{g_m \rightarrow \infty} \frac{g_m^2 \left(\frac{R_1 + R_2}{g_m^2} + R_2 / g_m \right)}{\frac{1}{g_m^2} + R_2 / g_m + R_2 R_3} = \frac{0}{R_2 R_3} = \boxed{0 = R_{in}}$$

$$\frac{V_o}{i_{in}} = \lim_{g_m \rightarrow \infty} \frac{g_m^2 R_L \left[R_3 (R_1 + R_2) + R_2 / g_m \right]}{g_m^2 \left[\frac{1}{g_m^2} + R_2 / g_m + R_2 R_3 \right]}$$

$$= \frac{R_L (R_3 (R_1 + R_2))}{R_2 R_3} = \boxed{R_L \left(1 + \frac{R_1}{R_2} \right) = \frac{V_o}{i_{in}}}$$




14

TUESDAY

MAY

2019

3b)

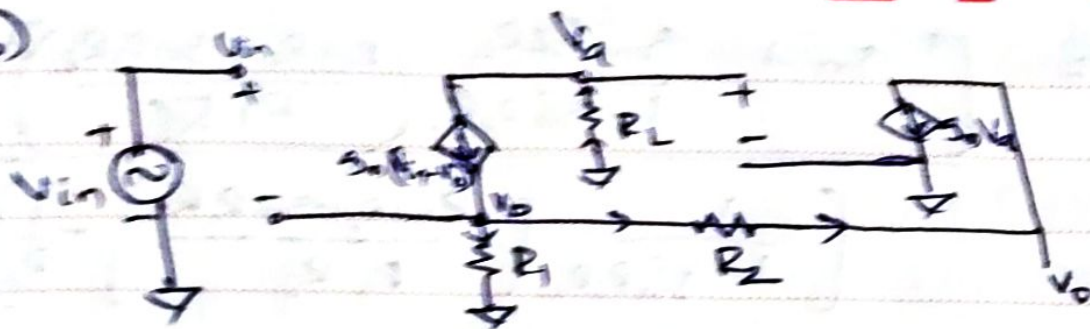

$$KCL \Rightarrow V_a = -g_m(V_{in} - V_b) R_L \quad \text{--- (1)}$$

$$KCL \Rightarrow V_b - V_o = g_m V_a R_2 \quad \text{--- (2)}$$

$$KCL \Rightarrow g_m(V_{in} - V_b) = \frac{V_b}{R_1} + \frac{V_b - V_o}{R_2}$$

$$\Rightarrow \boxed{g_m V_{in} + \frac{V_o}{R_2} = V_b \left[\frac{1}{R_1} + \frac{1}{R_2} + g_m \right]} \quad \text{--- (3)}$$

From (1) and (2),

$$\begin{aligned} V_b - V_o &= g_m R_2 (-g_m(V_{in} - V_b)) R_L \\ &= -g_m^2 R_2 R_L V_{in} + g_m^2 R_2 R_L V_b \end{aligned}$$

$$V_b(1 - g_m^2 R_2 R_L) = V_o - g_m^2 R_2 R_L V_{in}$$

$$V_b = \frac{V_o - g_m^2 R_2 R_L V_{in}}{1 - g_m^2 R_2 R_L}$$

$\xrightarrow{\text{Plug in (3)}}$

$$\Rightarrow g_m V_{in} + \frac{V_o}{R_2} = \frac{V_o - g_m^2 R_2 R_L V_{in}}{1 - g_m^2 R_2 R_L} \left[\frac{R_1 + R_2 + g_m R_1 R_2}{R_1 R_2} \right]$$

$$\Rightarrow V_{in} \left[g_m + \frac{g_m^2 R_2 R_L}{1 - g_m^2 R_2 R_L} \left[\frac{R_1 + R_2 + g_m R_1 R_2}{R_1 R_2} \right] \right]$$


$$= V_o \left[\frac{1}{1 - g_m^2 R_2 R_L} \left[\frac{R_1 + R_2 + g_m R_1 R_2}{R_1 R_2} \right] - \frac{1}{R_2} \right]$$

$$\begin{aligned}
 \frac{V_o}{V_{in}} &= \frac{\left[g_m + \frac{g_m^2 R_2 R_L}{1 - g_m^2 R_2 R_L} \left(\frac{R_1 + R_2 + g_m R_1 R_2}{R_1 R_L} \right) \right]}{\left[\frac{1}{1 - g_m^2 R_2 R_L} \left(\frac{R_1 + R_2 + g_m R_1 R_2}{R_1 R_2} \right) - \frac{1}{R_2} \right]} \\
 &= \frac{\left[g_m (1 - g_m^2 R_2 R_L) R_2 + g_m^2 R_2 R_L (R_1 + R_2 + g_m R_1 R_2) \right]}{R_1 + R_2 + g_m R_1 R_2 - R_1 (1 - g_m^2 R_2 R_L)} \\
 &= \frac{g_m R_2 - g_m^3 R_1 R_2^2 R_L + g_m^2 R_2 R_L (R_1 + R_2) + g_m^3 R_1 R_2^2 R_L}{R_2 + g_m R_1 R_2 + g_m^2 R_1 R_2 R_L}
 \end{aligned}$$

$$\boxed{\frac{V_o}{V_{in}} = \frac{g_m R_1 R_2 + g_m^2 R_2 R_L (R_1 + R_2)}{R_2 + g_m R_1 R_2 + g_m^2 R_1 R_2 R_L}}$$

$$\text{As } g_m \rightarrow \infty, \frac{V_o}{V_{in}} \rightarrow \frac{R_2 R_L (R_1 + R_2)}{R_1 R_L R_L} = \left(1 + \frac{R_2}{R_1} \right)$$

For V_{out} ,

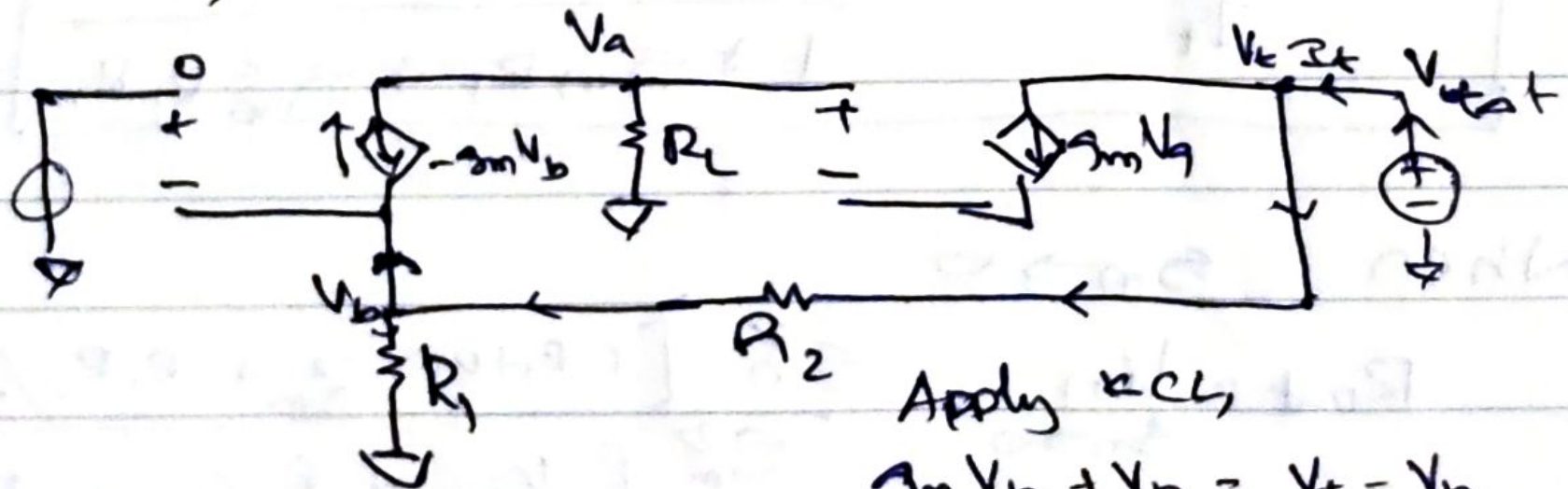

Apply KCL,

$$3mV_b + \frac{V_b}{R_1} = \frac{V_t - V_b}{R_2}$$

$$V_a = 3mV_b R_L$$

$$\Rightarrow V_b \left[3m + \frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{V_t}{R_2}$$

And, $\frac{V_E - V_B}{R_2} = I_{\text{test}} - g_m V_E$

$$\Rightarrow V_E - V_B = R_2 I_{\text{test}} - g_m^2 V_B R_L R_2$$

$$\Rightarrow V_B = \frac{V_E - R_2 I_{\text{test}}}{1 - g_m^2 R_L R_2}$$

from previous relation of V_B , we get

$$\frac{V_E - R_2 I_E}{1 - g_m^2 R_L R_2} \left[\frac{R_1 + R_2 + g_m R_1 R_2}{R_1 R_2} \right] = \frac{V_E}{R_2}$$

$$\Rightarrow V_E - R_2 I_E = \frac{(1 - g_m^2 R_L R_2) R_1}{R_1 + R_2 + g_m R_1 R_2}$$

$$\Rightarrow V_E \left[\frac{R_1 + R_2 + g_m R_1 R_2 + g_m^2 R_L R_1 R_2 - R_1}{R_1 + R_2 + g_m R_1 R_2} \right] = R_2 I_E$$

$$\Rightarrow V_E R_2 \left(\frac{1 + g_m R_1 + g_m^2 R_L R_1}{R_1 + R_2 + g_m R_1 R_2} \right) = R_2 I_E$$

$$\Rightarrow \boxed{R_{\text{out}} = \frac{V_E}{I_E} = \frac{R_1 + R_2 + g_m R_1 R_2}{1 + g_m R_1 + g_m^2 R_L R_1}}$$

When $g_m \rightarrow \infty$

$$R_{\text{out}} = \lim_{g_m \rightarrow \infty} \frac{g_m^2 \left[(R_1 + R_2)/g_m^2 + R_1 R_2/g_m^2 \right]}{g_m^2 \left[1/g_m^2 + R_1/g_m + R_1 R_L \right]}$$

$$= \frac{0}{R_1 R_L} \Rightarrow \boxed{R_{\text{out}} = 0}$$