




Mo Tu We Th Fr Sa Su

Date / /

Assignment - 4

D

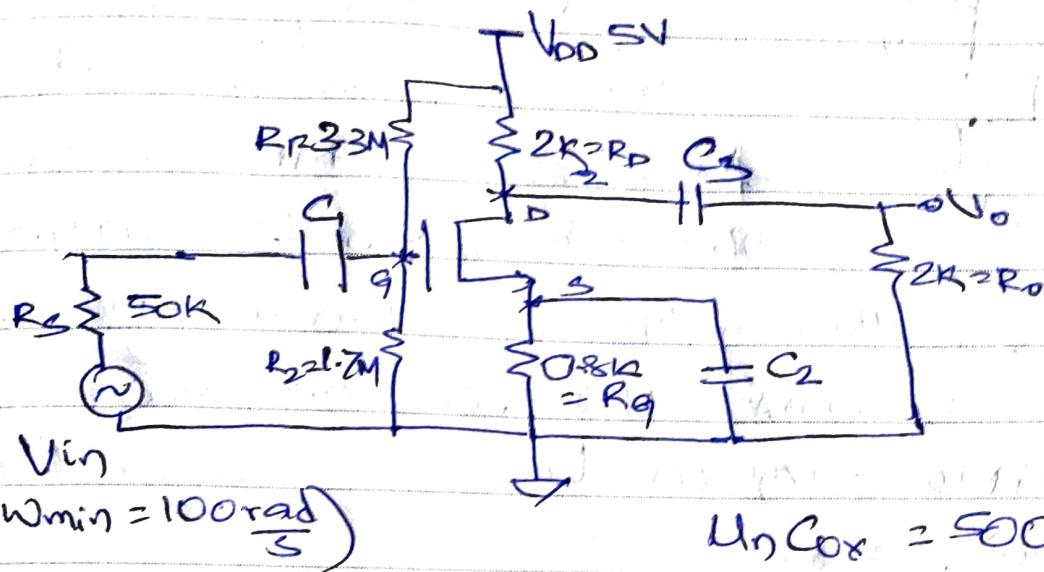

$$(W_{min} = 100 \frac{rad}{s})$$

$$U_{n,Cox} = 500 \text{ nA V}^{-2}$$

$$V_T = 0.7 \text{ V}$$

$$I_{DS} = 1 \text{ mA}$$

As we can see I_{DS} is 1mA, we get

$$V_S = 0.8 \text{ V} \times 1 \text{ mA} = 0.8 \text{ V}$$

$$V_D = 5 - 2 \text{ k} \times 1 \text{ m} = 3 \text{ V}$$

$$\Rightarrow V_{DS} = 2.2 \text{ V}$$

And assuming the d.c. biasing is done properly, we get

$$V_G = 5 \text{ V} \times \frac{1.7 \text{ M}}{1.7 \text{ M} + 3.3 \text{ M}} = 1.7 \text{ V}$$

$$(\boxed{V_G = 1.7 \text{ V}})$$

$$\Rightarrow V_{GDS} = 1.7 \text{ V} - 0.8 \text{ V}$$

$$\boxed{V_{GDS} = 0.9 \text{ V}}$$

$$\Rightarrow V_{GS} - V_T = 0.9 - 0.7 \\ = 0.2 \text{ V}$$



Mo Tu We Th Fr Sa Su

Date / /

As the $V_{DS} - V_T < V_{DS}$, the MOS is in saturation and

$$I_{DS} = \frac{W}{2L} C_{ox} W (V_{DS} - V_T)^2$$

$$1mA = 500\mu A \times \frac{W}{2L} \times \frac{1}{28}$$

$$\Rightarrow \boxed{\frac{W}{L} = 100}$$

(b) For C_1 , the $R_{eff1} = R_S + (R_1 || R_2)$

$$\Rightarrow R_{eff1} \times C_1 \geq \frac{1}{\omega_{min}} \Rightarrow R_{eff1} C_1 = \frac{10 \times 2\pi}{\omega_{min}}$$

$$\Rightarrow C_1 = \frac{10 \times 2\pi}{\omega_{min}(R_{eff1})} = \frac{10 \times 2\pi}{(10)(1172)(1000)} \\ \approx \frac{2\pi}{1172} \times 10^{-4} = 0.000853 \times 10^{-4} \text{ F} \\ = 2.853 \text{ nF} = 2.853 \text{ nF}$$


For C_2 , the $R_{eff2} = R_G$

$$\Rightarrow C_2 = \frac{10 \times 2\pi}{\omega_{min} R_{eff2}} = \frac{10 \times 2\pi}{(10)(0.8k)} = \frac{2\pi}{8} \text{ mF} \\ = 125 \text{ uF} \times 2\pi = 785.398 \text{ uF}$$

For C_3 , the $R_{eff3} = R_D + R_D$

$$\Rightarrow C_3 = \frac{10 \times 2\pi}{\omega_{min} R_{eff3}} = \frac{10 \times 2\pi}{100(4k)} = 0.25 \times 10^{-4} \\ = 25 \text{ uF} \times 2\pi = 157.0796 \text{ uF}$$

i) c) Incremental Picture:

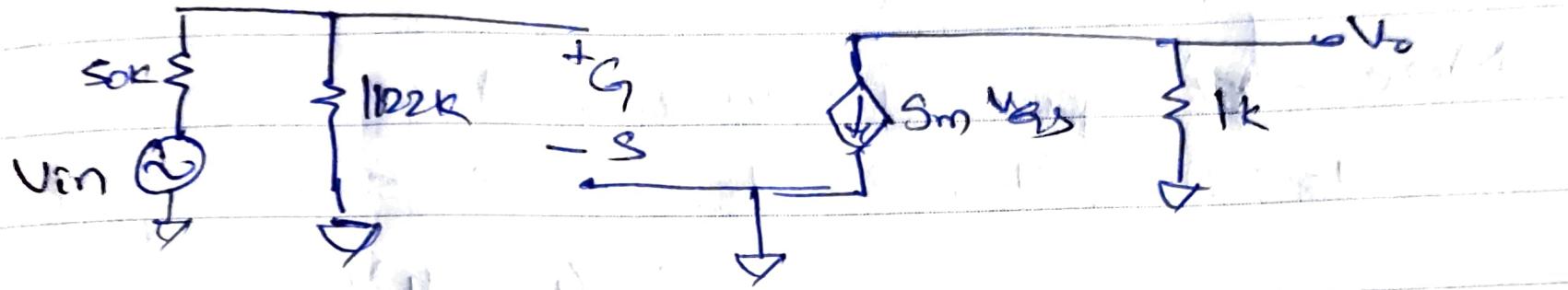

$$V_{GS} = Vin \frac{1122K}{1172K} = \frac{1122}{1172} Vin$$

$$V_d = -g_m V_{GS} \times 1K$$

$$\Rightarrow \frac{V_d}{Vin} = -g_m \times \frac{1122}{1172} \times 1K$$

And $g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) = \frac{2 I_{DS}}{V_{GS} - V_T}$

$$I_{DS} = 1mA \quad V_{GS} - V_T = 0.2V \Rightarrow g_m = \frac{2 \times 1m}{0.2} = 10^{-2}$$


$$\Rightarrow \frac{V_d}{Vin} = -10^{-2} \times \frac{1122 \times 10^3}{1172} = -9.57$$



Mo Tu We Th Fr Sa Su

Date / /

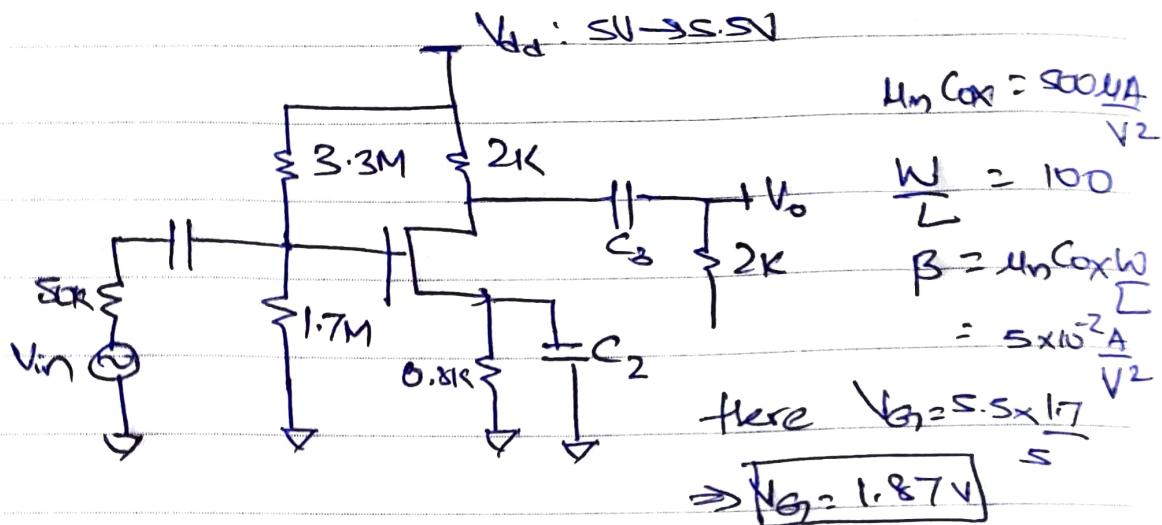1)d) V_{DD} is changed to 5.5V. New gain:



The gain we found has expression:

$$\text{Gain} = -g_m V_{GS} (R_D \| R_L)$$

And $I_{DS} = \frac{V_D}{R}$; $I_{DS} = \frac{\beta}{2} \left(\frac{V_{GS} - V_T}{\frac{V_D - V_S}{R}} \right)^2$

$$\Rightarrow \frac{V_D}{0.8 \times 10^2} = \frac{5 \times 10^{-2}}{2} (1.17 - V_S)^2$$

On solving quadratic we get $V_S = 0.9518$ (1)

but MOS is in saturation so $(V_S = 0.9518V)$ 1.438

Then $g_m = \beta (V_{GS} - V_T)$

$$= 500 \times 10^{-2} \times 100 (1.17 - 0.95)$$

$$= 1.1 \times 10^{-2}$$

Gain: $-g_m N_G \times \frac{1}{1k} = -10.12$

so the |Gain| increases from 9.5 to 10.12



Mo Tu We Th Fr Sa Su

Date _____

Ques) Now V_T changed from 0.7V to 0.8V

Then we have $V_D = \frac{5 \times 1.7}{3} = 1.7V$

$$V_S = I_{DS}(0.8k)$$

And $I_{DS} = \beta(V_{GS} - V_T)$

$$\Rightarrow \frac{V_S}{0.8k} = \frac{500 \times 10^6 \times 100}{2} (1.7 - V_S - 0.8)^2$$

$$\Rightarrow V_S = 20(0.9 - V_S)^2$$

$$\Rightarrow (20)V_S^2 - (20 \times 1.8 + 1)V_S + 20(0.9)^2 = 0$$

$$\Rightarrow V_S = 1.113 / 0.711, \text{ but if } V_S = 1.113, V_{GS} - V_T < 0$$

$$\Rightarrow V_S = 0.71139, 3m = \beta(V_{GS} - V_T)$$

Then $3m = 0.945 \times 10^{-2}$

Then Gain = $-3m V_{GS} \times 1k$

$$= -(0.71139 \times 10^{-2} \times 0.3866 \times 10^3)$$


$$= -9.3423$$

Hence the [gain] has reduced from 9.58 to 9.34.



Mo Tu We Th Fr Sa Su

Date / /

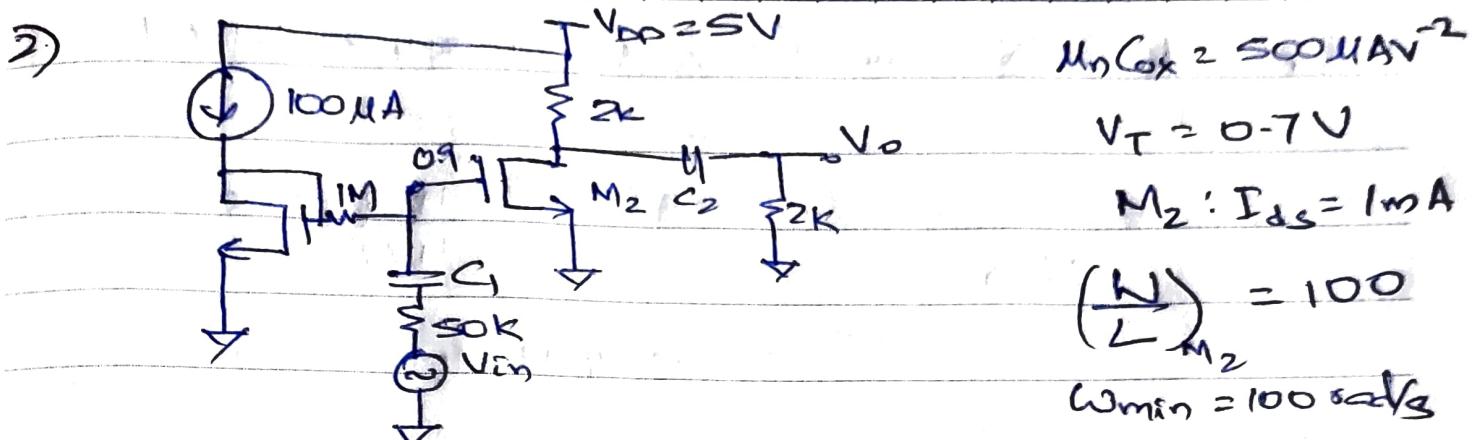

a) For M_2 , $I_{ds} = \frac{4 \pi C_{ox} W}{2L} (V_{GS} - V_T)^2$

$$\Rightarrow 10^{-3} = \frac{500 \times 10^{-6}}{2} \times 100 \times (V_{GS} - 0.7)^2$$

$$\Rightarrow \frac{1}{5} = V_{GS} - 0.7 \Rightarrow V_{GS} = 0.9V$$

And $V_{DS} = 5 - 2k \times 1mA \Rightarrow V_{DS} = 3V$

Now Coming M_1 , we have $I_{ds} = 100mA$

$$\Rightarrow 100mA = \frac{500 \mu}{2} \left(\frac{W}{L}\right)_{M_1} (0.9 - 0.7)^2$$

$$\Rightarrow \boxed{\left(\frac{W}{L}\right)_{M_1} = 10} \quad V_{GS} = V_{DS} = 0.9V$$

b) For C_2 , we can say from incremental picture

$$R_{eff} = R_{ot} \| R_L = \frac{2k}{2+1} = 4k$$

$$\Rightarrow C_2 = \frac{10 \times 2\pi}{\omega_{min} R_{eff}} \Rightarrow \frac{10}{100 \times 4k} \Rightarrow \boxed{25 \text{ nF}}$$


$$\Rightarrow C_2 = 157.0796 \text{ nF}$$



Mo Tu We Th Fr Sa Su

Date _____

And for C_1 ,

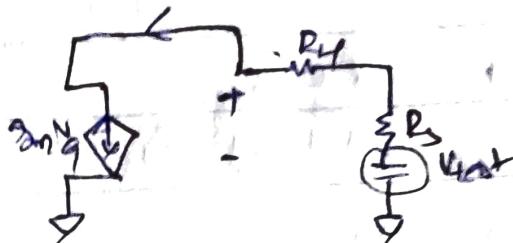

$$I = \frac{3mV_{in}}{1 + 3mR_4}$$

$$\Rightarrow R_{eff} = \left(\frac{1}{3m} + R_4 \right) + R_3$$

For $3m$, we have


$$3m = 500 \times 10^3 \times 10 \times (0.2) = 1m\Omega^{-1}$$

$$\Rightarrow R_{eff} = 1k + 50k + 1M \approx 1M$$

$$C_1 = \frac{10 \times 2\pi}{10m R_{eff}} = \frac{10 \times 2\pi}{10 \times 10^6} = 0.14F \times 2\pi$$

$$= 0.628nF$$

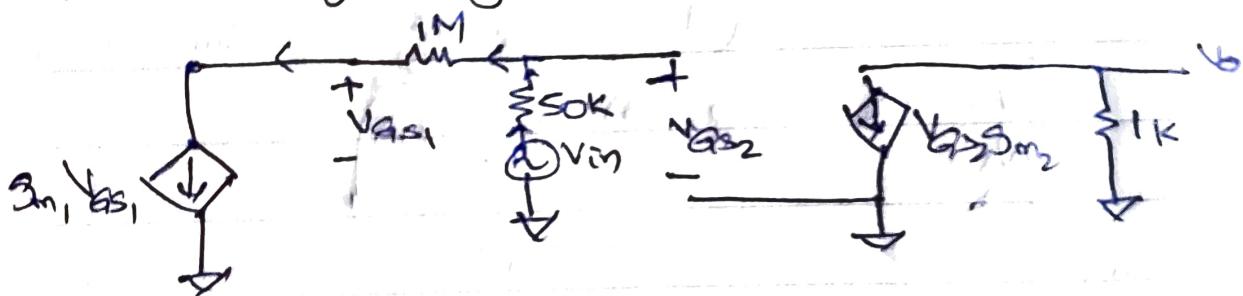c) Small signal gain, the incremental picture



$$\text{For } M_1 \text{ model: } \frac{V_{in} - V_{as1}}{1M + 50k} = 3mV_{as1}$$

$$50k \ll 1M$$

$$\Rightarrow V_{in} - V_{as1} = 1M \times 3mV_{as1}$$

$$\Rightarrow V_{as1} = \frac{V_{in}}{1 + 3m(1M)}$$

$$\Rightarrow I = V_{in} - \frac{V_{in}}{1 + 3m(1M)} = \frac{V_{in}}{1M}$$

$$\Rightarrow I = \frac{3m}{1 + 3m(1M)} V_{in}$$



Mo	Tu	We	Th	Fr	Sa	Su
----	----	----	----	----	----	----

Date / /

For $V_{AS_2} = V_{in} - SOK \left(\frac{V_{in} 3m_1}{1 + 3m_1 M} \right)$

$$= V_{in} \left(1 - \frac{SOK 3m_1}{1 + 3m_1 M} \right)$$

$$V_o = -V_{AS_2} 3m_2 K$$

$$\Rightarrow \frac{V_o}{V_{in}} = - \left(1 - \frac{SOK 3m_1}{1 + 3m_1 M} \right) 3m_2 (K)$$

For a fair approximation $1 + 3m_1 M \approx 3m_1 (1M)$

$$\Rightarrow \frac{V_o}{V_{in}} \approx - \left(1 - \frac{SOK 3m_1}{1M 3m_1} \right) 3m_2 (1K)$$

$$\approx - \left(1 - \frac{SOK \times 10^3}{10^6 \times 10^3} \right) 3m_2 (1K)$$

$$\Rightarrow \boxed{\frac{V_o}{V_{in}} \approx - (0.95) 3m_2 (1K)}$$

$$3m_2 = \frac{2 I_{DS}}{(V_{DS} - V_T)} = \frac{2 \times 1mA}{(0.9 - 0.7)} = \frac{2 \times 10^{-3}}{2 \times 10^{-1}} = 10^2 \Omega$$

$$\Rightarrow \frac{V_o}{V_{in}} \approx - (0.95) 10^{-2} (1K)$$

$$V_{in} \approx \boxed{-9.5}$$



Mo Tu We Th Fr Sa Su

Date / /

2) Now it is said $V_{OP} : 5V \rightarrow 5.5V$

From the gain formula we brought we have

$$\frac{V_o}{V_{in}} = - \left(1 - \frac{s_0 k g_{m1}}{1 + g_{m1} \times IM} \right) g_{m2} (1k)$$
$$\approx - (0.95) g_{m2} (1k)$$

$$\text{And } g_{m2} = \beta_2 (V_{G2} - V_{S2} - V_{T2}) \\ = \beta_2 (V_{G2} - V_{T2}) \quad (\because V_{S2} = 0)$$

But in M₁, (current mode biased), the I_{DS} and β_1 are unchanged making $V_{GS2} = V_{G2}$ to remain same. and as current through IM is 0A, the $V_{G1} \approx V_{GS1}$. When $V_{G2} \approx V_{T2}$ remain unchanged, (I_{DS}) and g_{m2} also remain same and so is the gain which is

$$\boxed{\frac{V_o}{V_{in}} \approx -9.5}$$

When compared to (1), this is different as in (1), the V_G is being directly controlled by voltage driven source divider. But here the current is maintained by a current source and V_G can still remain the same.

∴ We have Gain: $\rightarrow (0.95) \beta m_2 (1K)$

$$\begin{aligned} \beta m_2 &= \beta_2 (V_{G_2} - V_{T_2} - V_T) \\ &= \beta_2 (V_{G_2} - V_{T_2}) \end{aligned}$$

Case (i): $V_T \rightarrow 0.7V$ to $0.8V$

V_{G_2} constant $0.7V$

In M₁, I_{DS} is maintained to $100mA$, hence

$$\begin{aligned} 100mA &= \frac{500 \times 10^6 \times 100}{(V_{G_1} - V_T)^2} (V_{G_1} - V_{T_1})^2 \\ \Rightarrow 0.2 &= V_{G_1} - V_{T_1} \\ \Rightarrow V_{G_1} &= 0.2 + V_{T_1} = 0.2 + 0.8 = \cancel{1V} \\ &= 1V \end{aligned}$$

And as we saw $V_{G_1} \approx V_{G_2}$, we get

$$\begin{aligned} \beta m_2 &= 500 \times 10^6 \times 100 (1 - 0.7) \\ &= 5 \times 10^2 \times 0.3 = 1.5 \times 10^3 A \end{aligned}$$

$$\begin{aligned} \text{Gain} &= 10 \times 0.95 \times 1.5 \times 10^3 < 1K \\ &= -14.25 \end{aligned}$$

The |Gain| increased from 9.5 to 14.25

Case (ii): $V_{T_1} \rightarrow \text{const } 0.7V$

$V_{T_2} \rightarrow 0.7V$ to $0.8V$

We still have $V_{G_1} = V_{G_2} = 0.9V$

$$\begin{aligned} \Rightarrow \beta m_2 &= \beta_2 (V_{G_2} - V_{T_2}) \\ &= 5 \times 10^2 (0.7 - 0.8) \\ &= 5 \times 10^2 \times 0.1 \end{aligned}$$



Mo	Tu	We	Th	Fr	Sa	Su
----	----	----	----	----	----	----

Date / /

$$\text{Gain} := -0.95 \times 5 \times 10^3 \times 10^3 = -4.75$$

The $|V_{out}|$ has reduced from 9.5 to 4.75.

Case (ii): $V_{T_1} \Rightarrow 0.7V$ to 8V

$V_{T_2} \Rightarrow 0.7V$ to 8V


Then from earlier analysis we get

$$V_{A2} = 0.9V + 0.1V \Rightarrow (V_{A2})_2 = 0.2V$$

$$V_{T_2} = 0.7V + 0.1V \quad \text{as before}$$

As $(V_{A2})_2$ remains same, so does $g_m)_2$, so does the gain. Then $\frac{V_o}{V_{in}} = -9.5$.

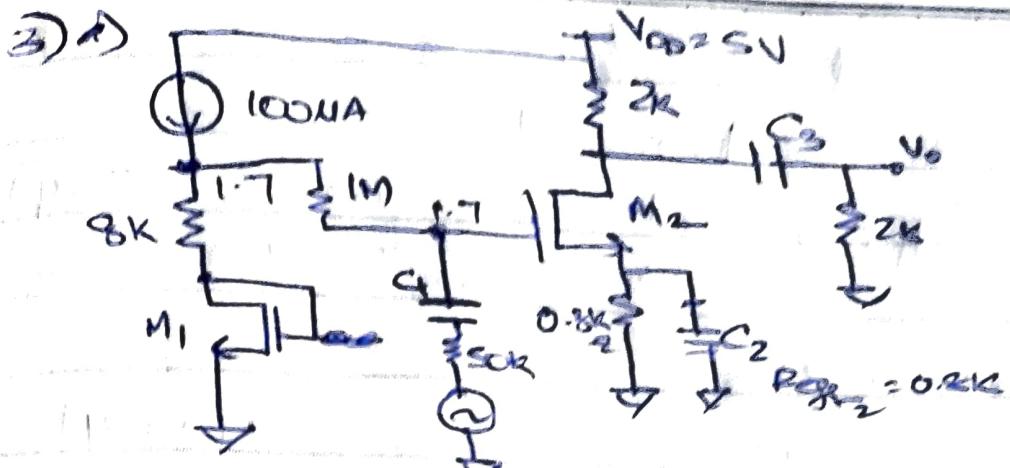→ When compared to problem (i), the control of source supply voltage has been removed, and swings in gain for small change in threshold voltages are scaling up more.



For M_1 , the Ide
current can't flow
through $R_{high} = 1M$

$$N_{D\sigma} = 1.7 - 1000 \times 8 \times 10^{-12} = 1.7 - 0.8 = 0.9 \text{ N/V}$$

$$(V_{AB})_{M_1} = (V_{AB})_{H_1} = 0.9 \text{ V}$$

$$-A_m \& 100\text{ MA} = \frac{500 \times 10^6 \times (\frac{W}{L})_{m_1}}{2} \times (0.9 - 0.7)^2$$

$$\Rightarrow \frac{w}{L} = 10$$

$$y_{D3} = 5 - 2x \quad (y \neq 4) \Rightarrow 3$$

$$(V_{DS})_{M_2} = 2.2V$$

$$\text{And } (N_{A_2})_{M_2} = \frac{0.8V}{2 \times 10^{-3}} = 800 \times 10^3 \text{ A}^{-1}$$

$$\Rightarrow N_{\text{eff}} n_2 - 0.7 \approx 0.2$$

$$\Rightarrow \text{Na}_2\text{H}_2 = 0.9$$

b) Now for effective caps, we can observe that C_3 and C_2 are unaffected by the current of source at drain hence remain same.


$$\Rightarrow C_2 = \frac{100 \times 2\pi}{100 \times 0.3 \times 1k} = 78\mu F$$

For C1, look into the Ray picture



Mo	Tu	We	Th	Fr	Sa	Su
----	----	----	----	----	----	----

Date / /

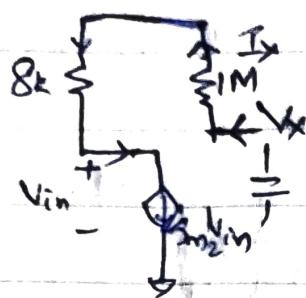

$$\frac{V_x - V_{in}}{8k + 1M} = 3mV_x$$

$$\Rightarrow V_{in} = \frac{V_x}{1 + 3m(8k+1M)}$$

$$\Rightarrow I_x = \frac{3mV_x}{1 + 3m(8k+1M)}$$

$$\Rightarrow R_x = \frac{1}{3m} + 8k + 1M$$

\therefore Eff. resistance : $R_3 = R_x + R_S$

$$= \frac{1}{3m} + 8k + 1M + 50k$$

Now $3m^2 = \frac{500 \times 10^{-6} \times 10^3 (0.9 - 0.7)}{10} = 5 \times 10^{-3} \times 0.2$

$$= 10^{-3}$$

$$\Rightarrow R_{eff,3} = 1k + 8k + 1M + 50k = 1M + 59k$$


Though $R_{eff,3}$ has increased, the IMR is still dominant and can nearly be approximated to it which results, even C_F to remain same

i.e $C_F = \frac{10^{-20}}{1000 R_{eff,3}} \approx 0.1 \mu F \times 2\pi =$

And $3m_1 = \frac{500 \times 10^{-6} \times 100}{10} (0.9 - 0.7) = 10^{-2}$

2.C) Incremental Picture:

Date _____

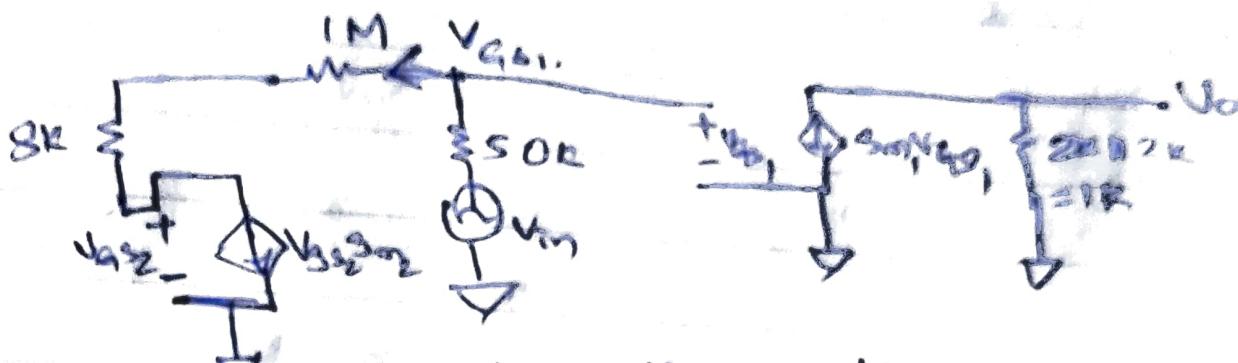

$$\frac{V_{in} - V_{GS1}}{50K} = \frac{V_{GS1} - V_{GS2}}{1M + 8K} = V_{GS2} 3m_2$$

$$\Rightarrow V_{GS1} = V_{GS2} (1 + 3m_2 (1M + 8K)) \Rightarrow V_{GS2} = \frac{V_{GS1}}{1 + 3m_2 (1M + 8K)}$$

$$\Rightarrow V_{in} = V_{GS1} \left(1 + \frac{3m_2 50K}{1 + 3m_2 (1M + 8K)} \right)$$

$$\Rightarrow V_{GS1} = \frac{V_{in}}{1 + \frac{3m_2 50K}{1 + 3m_2 (1M + 8K)}}$$

$$V_o = -(1K) 3m_2 V_{GS1}$$

$$= -(1K) 3m_2 \frac{V_{in}}{1 + \frac{3m_2 50K}{1 + 3m_2 (1M + 8K)}}$$

$$\Rightarrow \frac{V_o}{V_{in}} = -\frac{(1K) 3m_2}{1 + \frac{3m_2 (50K)}{1 + 3m_2 (1M + 8K)}}$$



Mo	Tu	We	Th	Fr	Sa	Su
----	----	----	----	----	----	----

Date / /

We have $3m_2 = 10^3$ and $3m_1 = 10^2$. then


we can see that $1 + 3m_2(1M+8k) \approx 3m_2(1M+8k)$

Then,

$$\frac{V_o}{V_{in}} = - \frac{(1K) 3m_1}{1 + \frac{3m_2(500k)}{3m_2(1M+8k)}}$$
$$= - \frac{(10k)(10^2)}{1M+8k + 500k} (1M+8k) \approx \frac{(1M+8k)(10)}{1M+58k}$$

$$\approx -9.527$$

3) d)

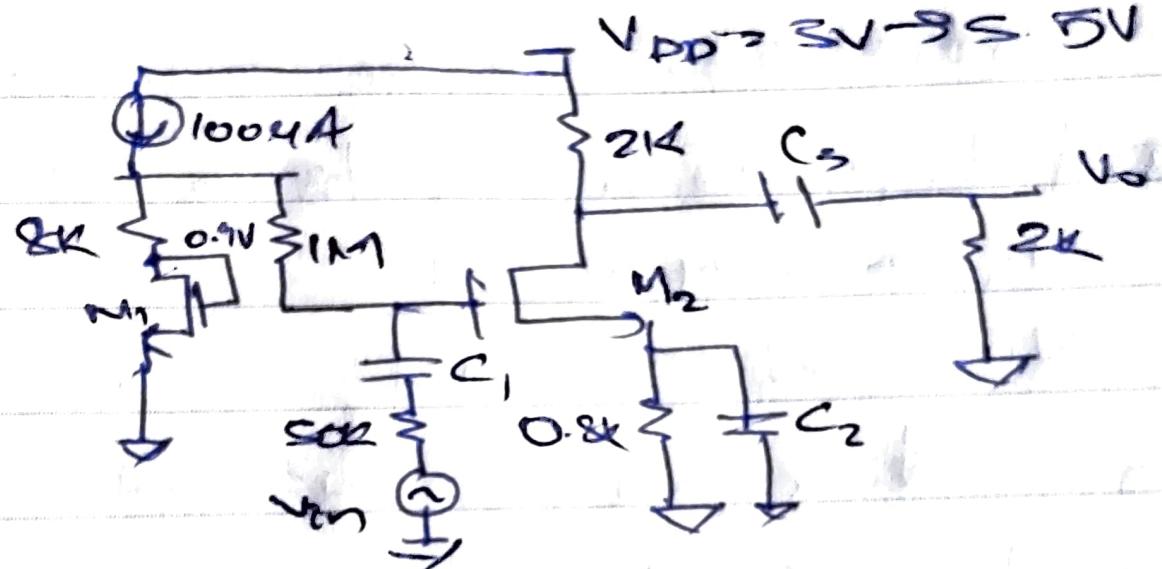

Gain \approx

$$= \frac{(1M + 8k) \times g_{m2}}{1M + 8k} \times 1k$$

Now, V_{DD} is changed from 5V to 5.5V.

$$\Rightarrow V_{S2} = 0.8k \cdot g_{m2}$$

$$V_{S2} = V_{G1} + 8k \times 100mA$$

$$= 0.9V + 0.8V = 1.7V$$

Continue:

3) d) Gain :
$$\frac{-(M+8k)}{(IM+58k)} \times 1K \times \boxed{\beta_{m2}} \rightarrow \text{deciding factor}$$

$$I_{m2} = B_2 (V_{GS2} - V_{T2}) = B_2 (V_{G2} - V_{S2})$$

Change in gain: $\Delta g_f = B_2 (\Delta V_{G2} - \Delta V_{S2})$

$$I_{DS} = \frac{B}{2} (V_{G2} - V_{S2} - V_{T2})^2 = \frac{V_{DS2}}{0.8k}$$

$$\Rightarrow \frac{\Delta V_{S2}}{0.8k} = \frac{B}{2} (2)(V_{G2} - V_{S2} - V_{T2}) (\Delta V_G - \Delta V_{S2})$$

But as we saw earlier $\Delta V_{G2} = 0$ because the current biased Mos maintaining the voltage.

$$\Rightarrow \Delta V_{S2} \left[\frac{1}{0.8k} + B (V_{G2} - V_{S2} - V_{T2}) \right] = 0$$

$$\Rightarrow \Delta V_{S2} = 0 \Rightarrow \Delta \text{Gain} = 0$$



Mo Tu We Th Fr Sa Su

Date / /

Hence gain is same - 9.527. This case is very similar to the Case (2) problem. Though here there is a resistance $8k\Omega$ on top of M_1 , the V_g relative increased from Case (2) but remains constant. And form (2) , the resistance added at source though has dependence on I_{DS} , for V_s , the change in V_s is again dictated by the change in V_g . So in effect, the new resistance doesn't change the control for V_{DD} on gain.

③ (2) Small signal gain:

a) $V_{TN_1} = 0.7 \rightarrow 0.8V$ and $V_{TN_2} = 0.7V$

$\therefore I_{DS} = 100mA$, then

$$\Rightarrow I_{DS_1} = \frac{B_1}{2} (V_{GS_1} - V_{T_1})^2 \Rightarrow 100mA = \frac{500 \times 10^6 \times 10^{-6}}{2} (V_{GS_1} - V_{T_1})^2$$

$$\Rightarrow V_{GS_1} - V_{T_1} = \frac{1}{5} \Rightarrow V_{GS_1} = 0.8 + 0.2 = 1V$$

Then $V_{G_2} = V_{GS_1} + 8k\Omega(100mA)$

$$= 1V + 8 \times 10^3 \times 10^{-4} = 1.8V$$

$$V_{S_2} = I_{DS_2} (0.8k)$$

$$\Rightarrow I_{DS_2} = \frac{B_2}{2} (V_{GS_2} - V_{T_2})^2$$

$$\Rightarrow \frac{V_{S_2}}{0.8k} = \frac{500 \times 10^6 \times 100}{2} (V_{G_2} - V_{S_2} - V_{T_2})^2$$



Mo	Tu	We	Th	Fr	Sa	Su
----	----	----	----	----	----	----

Date

$$\Rightarrow V_{S2} = \frac{0.8 \times 5 \times 10^2 \times 10^2}{20} (11.8V - 1V_{S2} - 0.7)^2$$

$$\Rightarrow V_{S2} = 20(1.1 - V_{S2})^2 \rightarrow 20V_{S2}^2 - (2(20 \times 1.1) + 20)V_{S2}$$

$$\Rightarrow V_{S2} = 1.3608 \boxed{0.8891}$$

(This is the condition \rightarrow For saturation)

Purpose.

$$\text{then } I_{D2} = B(V_{GS2} + V_{T2}) \\ = 500 \times 10^6 \times 100 (1.8 - 0.8891 - 0.7) \\ = 5 \times 10^{-2} \times 0.210 = 1.054 \times 10^{-2}$$

$$\text{Gain : } -\frac{(1M+8k)}{(1M+5k)} \times 1.054 \times 10^{-2} \times 1K = -10.0418$$

\therefore The gain had increased from 9.52 to 10.0418 on increasing V_T of M₂.

$$3) \text{ c) } V_{T1} : 0.7V \quad V_{T2} : 0.8V$$

$$\text{Now again } V_{GS1} - V_{T1} = 0.2 \Rightarrow V_{GS} = 0.9V$$

$$\Rightarrow V_{GS2} = V_{GS1} + 0.8V = 1.7V$$

$$V_{S2} = I_{D2} (0.8k)$$

$$\Rightarrow I_{D2} = \frac{B_2}{2} (V_{GS2} - 0.8)^2$$

$$\Rightarrow V_{S2} = \frac{0.8 \times 5 \times 10^2 \times 100}{20} (1.7 - V_{S2} - 0.8)^2$$

$$\Rightarrow V_{S2} = 20 (0.9 - V_{S2})^2$$

$$\Rightarrow V_{S2} = 20(0.9 - V_{S2})^2$$

$$\Rightarrow 20(V_{S2})^2 - \underbrace{(2(20)(0.9) + 1)V_{S2}}_{37} + \underbrace{20(0.9)^2}_{0.81} = 0$$

$$16.2$$

$$\Rightarrow V_{S2} = 1.1386 \text{ (approx)} \boxed{0.71}$$

↳ saturation region

$$3m_2 = 500 \times 10^{-3} \times 108 \times (0.9 - 0.71)$$

$$= 0.945 \times 10^{-2}$$

$$\text{Gain: } -\left(\frac{M+3K'}{M+58K}\right) 3m_2 (1+)$$

$$= -9.0034$$


The gain has reduced from 9.52 to 9.0034.

$$③ (c) V_{T1}: 0.7 \rightarrow 0.8, V_{T2}: 0.7 \rightarrow 0.8$$

Then, $V_{S2} - V_{T2} \Rightarrow$ will have no difference as V_{T1} changes V_{S2} to move from 0.7 to 1V and V_{T2} change from 0.7 to 0.8 making the effective difference.

→ In totality (2) & (3) are almost same, the gate voltage being operated is changed, rest remain the same including comparison from (1) Case.

④ Small signal gain, incremental picture

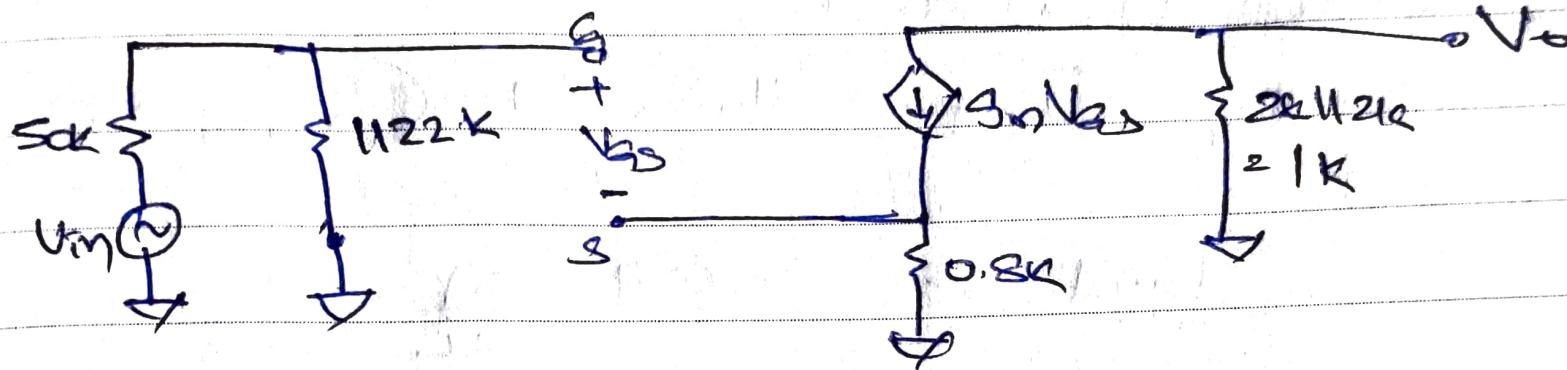

$$g_m = \frac{4 \pi C_{ox} W}{L} (V_{GS} - V_T)^{\frac{1}{2}} = \frac{800 \times 10^{-6}}{100 \times 10^{-2}} \times 10^{-2} = 1 \times 10^{-2}$$

$$\text{And } V_g = \frac{1122k}{1172k} V_{in} \text{ and } V_s = 0.8k \times g_m V_{GS} \\ = 0.8k \times 10^{-2} \times V_{GS} \\ V_s = 8 V_{GS}$$

$$\Rightarrow V_{GS} = \frac{1122}{1172} V_{in} - 8 V_s \Rightarrow V_{GS} = \frac{1122}{1172} \times \frac{V_{in}}{9}$$

$$\Rightarrow V_d = -g_m V_{GS} (1k) = -10^{-2} \times \frac{1122 \times V_{in} \times 10^{-3}}{1172 \times 9} \\ \Rightarrow \frac{V_d}{V_{in}} = -\frac{11220}{1172 \times 9} = -1.063$$