




Mo	Tu	We	Th	Fr	Sa	Su
----	----	----	----	----	----	----

Assignment-2

Date / /

1) Given 3-terminal device:

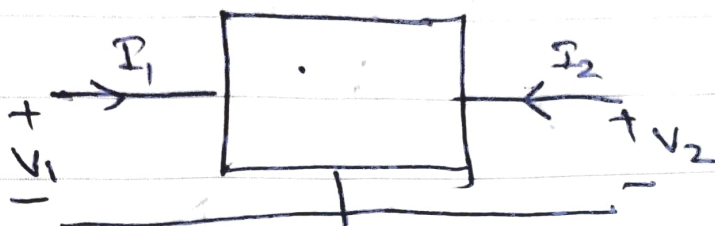


$$I_1 = \alpha V_1$$


$$I_2 = B V_1^2 + \gamma V_2$$

α, B, γ are constants

(i) Input characteristics:

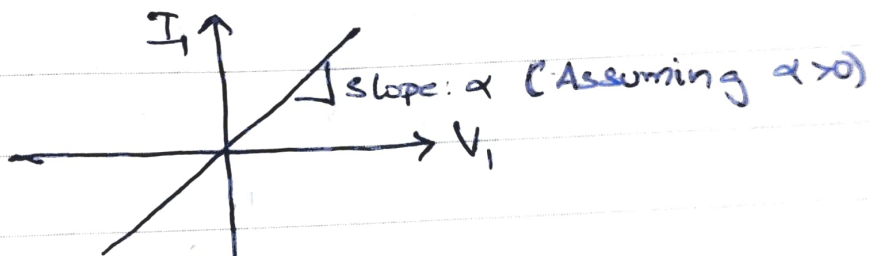

(ii) Output Characteristics:

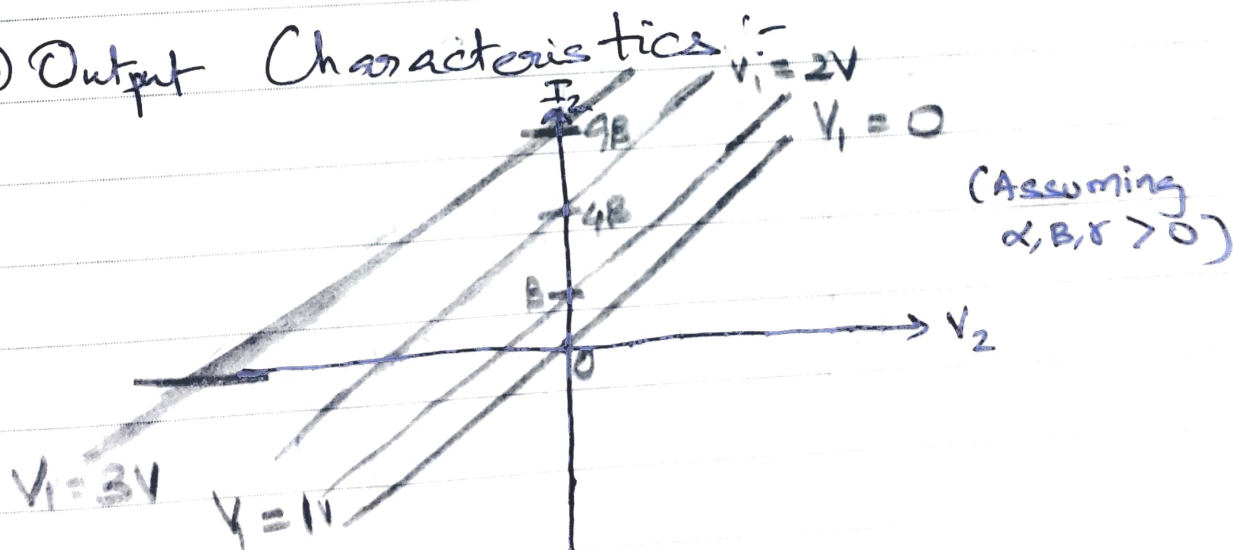

1) b) By Tellegen's theorem, we have
if $\sum_{k=1}^N V_k I_k \geq 0$, then system is Passive.



Mo	Tu	We	Th	Fr	Sa	Su
----	----	----	----	----	----	----

Date / /

$$\begin{aligned}\Rightarrow V_1 I_1 + V_2 I_2 &= V_1 (\alpha V_1) + V_2 (\beta V_1^2 + \gamma V_2) \\&= \alpha (V_1^2) + \beta V_1^2 V_2 + \gamma V_2^2 \\&= V_1^2 (\alpha + \beta V_2) + \gamma V_2^2 \\&= \gamma V_2^2 + (\beta V_1^2) V_2 + V_1^2 \alpha\end{aligned}$$

The device is active or passive depending on the constants α, β, γ . By taking $\alpha, \beta, \gamma > 0$, for the device to be passive we want $\gamma V_2^2 + (\beta V_1^2) V_2 + V_1^2 \alpha > 0$
 \rightarrow This can be ensured by making $\Delta < 0 \Rightarrow (\beta V_1^2)^2 < 4\gamma V_1^2 \alpha$
i.e. $\beta^2 V_1^2 < 4\gamma \alpha \Rightarrow V_1^2 < 4\gamma \alpha / \beta^2 \Rightarrow \frac{2\sqrt{\gamma \alpha}}{\beta} < V_1 < \frac{2\sqrt{\gamma \alpha}}{\beta}$
Then the device is assured to be passive.

By changing the constants, it can be active in certain operating region.

1) c) The incremental y-parameters when the device is op. at (V_1, V_2) is

$$y = \begin{bmatrix} \partial i_1 / \partial v_1 & \partial i_1 / \partial v_2 \\ \partial i_2 / \partial v_1 & \partial i_2 / \partial v_2 \end{bmatrix}$$

$$i_1 = \alpha V_1$$

$$i_2 = \beta V_1^2 + \gamma V_2$$


$$\Rightarrow y = \begin{bmatrix} \alpha & 0 \\ 2\beta V_1 & \gamma \end{bmatrix}$$



Mo Tu We Th Fr Sa Su


Date

2) Given,

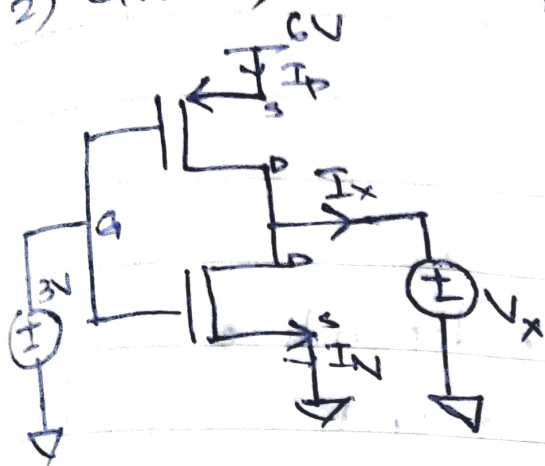

PMOS: $(V_{TP}) = 1V$ $\mu_p C_{ox} = 100 \mu A/V^2$
 $W/L = 3$ $V_{SG} = 6 - 3 = 3V$
 $V_{SD} = 6 - V_x$

NMOS: $|V_{TN}| = 1V$ $\mu_n C_{ox} = 300 \mu A/V^2$
 $W/L = 1$ $V_{GS} = 3V$
 $V_{DS} = V_x$

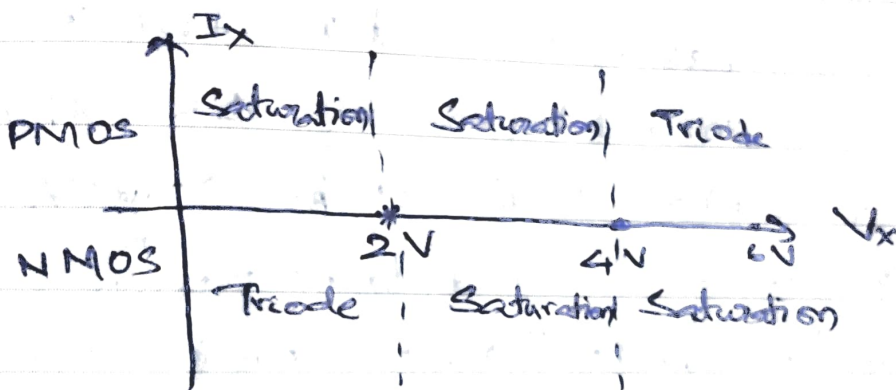


Hence, we will find the triode and saturation currents.

NMOS:

- Saturation: $I_{DS}^N = \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2$
 $= \frac{300 \times 1}{2} (2)^2 = 600 \mu A$
- Triode Region: $I_{DS}^N = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right]$
 $= 300 \times 1 \times \left[2V_{DS} - \frac{V_{DS}^2}{2} \right]$
 $= 150 \times V_x (4 - V_x)$

PMOS:

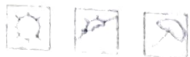- Saturation: $I_{SD}^P = \mu_p C_{ox} \frac{W}{2L} (V_{SG} - V_T)^2$



Mo	Tu	We	Th	Fr	Sa	Su
----	----	----	----	----	----	----

Date / /

$$\Rightarrow I_{SD}^P = 100 \times \frac{3}{2} \times (2)^2 = 600 \mu A$$

• Triode Region: $I_{SD}^P = \mu_{eff} C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{SD} - \frac{V_{SD}^2}{2} \right]$

$$\begin{aligned} \Rightarrow I_{SD}^P &= 100 \times 3 \left[(2)(6 - V_x) - \frac{(6 - V_x)^2}{2} \right] \\ &= 300 \times (6 - V_x) \times \left(2 - \frac{(6 - V_x)}{2} \right) \\ &= 300 \times (6 - V_x) \times \left(\frac{4 - 6 + V_x}{2} \right) \\ &= \frac{300}{150} \times (6 - V_x) \times \frac{(V_x - 2)}{2} = 150 (6 - V_x) (V_x - 2) \end{aligned}$$

Now, when


• $0 \leq V_x \leq 2V$: $I_x = I_{SD}^P(\text{sat}) - I_{DS}^N(\text{triode})$

$$\begin{aligned} \Rightarrow I_x &= 600 \mu A - 150 \times V_x (4 - V_x) \\ &= (600 - 600 V_x + 150 V_x^2) \mu A \end{aligned}$$

• $2V \leq V_x \leq 4V$: $I_x = I_{SD}^D(\text{sat}) - I_{DS}^N(\text{sat})$
 $= 600 \mu A - 600 \mu A = 0$

• $4V \leq V_x \leq 6V$: $I_x = I_{SD}^D(\text{triode}) - I_{DS}^N(\text{sat})$
 $= 150 (6 - V_x) (V_x - 2) - 600 \mu A$


∴ Plot is :

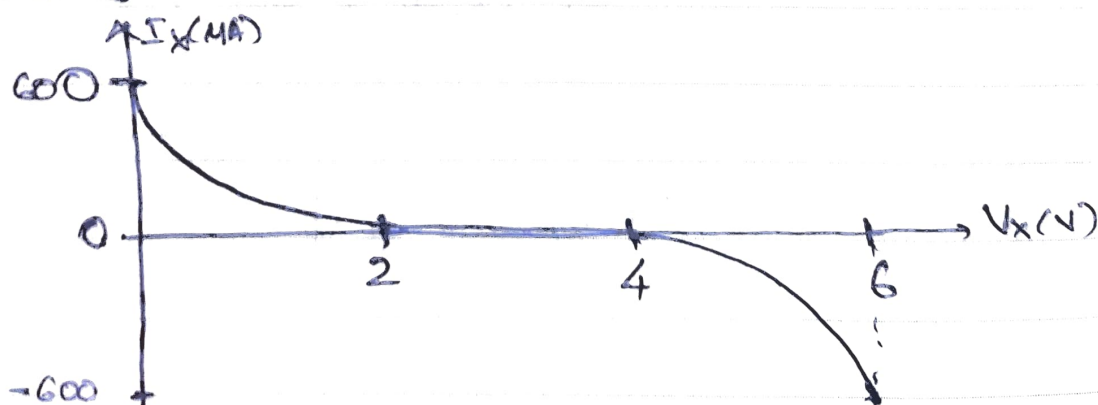



Given MOS parameters are

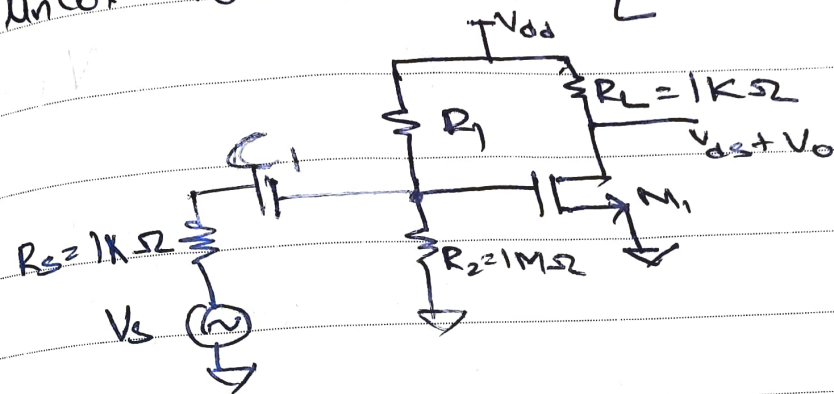
$$\mu_n C_{ox} = 100 \mu A/V^2, \quad \frac{W}{L} = 500, \quad V_T = 1V$$



We want R_1 and V_{DD} such that,

$$* (Gain) = g_m R_L = \frac{V_o}{V_s} = 10 \quad * V_{DS}|_{DC} = 5V$$

For D.C operation,

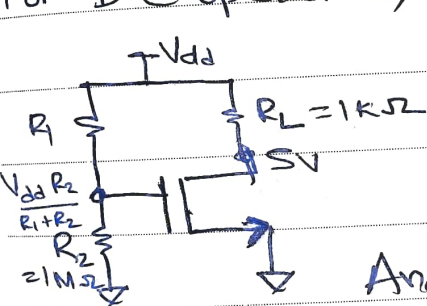

$$I_{DS} = \frac{V_{DD} - 5}{1K\Omega}$$

$$V_{GS} = \frac{V_{DD} R_2}{R_1 + R_2}$$

$$V_{GS} = \frac{V_{DD} (1M)}{R_1 + (1M)}$$

And we have,

$$g_m (1K\Omega) = 10 \Rightarrow g_m = 10m$$

And taking saturation,

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$$

$$\Rightarrow 10 \times 10^{-3} = 5 \times 10^{-2} (V_{GS} - 1)$$

$$\Rightarrow V_{GS} = \frac{6}{5} V$$

$$\text{And, } I_{DC} = \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2$$



Mo	Tu	We	Th	Fr	Sa	Su
----	----	----	----	----	----	----


Date / /

$$\Rightarrow \frac{V_{dd} - 5}{1K} = \frac{5 \times 10^{-2}}{2} \left(\frac{C_1}{5} - 1 \right)^2$$

$$\Rightarrow V_{dd} - 5 = 10^3 \times \frac{5}{2} \times 10^{-2} + \frac{1}{25} = 1 \Rightarrow V_{dd} = 6V$$

Hence $\frac{C_1}{5} = \frac{R_1 (1M)}{R_1 + (1M)} \Rightarrow R_1 + 1M = 5M$
 $\Rightarrow R_1 = 4M \Omega$

(b) For the incremental picture,

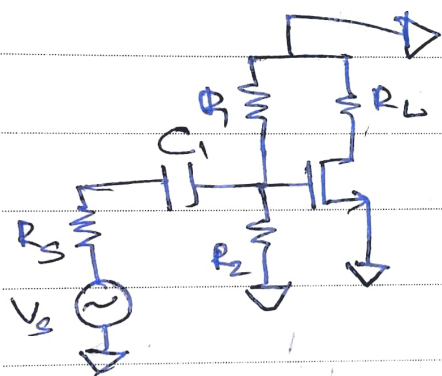

For finding the time constant associated with capacitor, we have

$$\Rightarrow R_{eff} = R_3 + (R_1 \parallel R_2)$$


$$= 1K + \frac{4M}{5}$$

$$= 801K \Omega$$

And for maintaining large enough discharge time, we have, $R_{eff} C_1 \gg \frac{1}{\omega_1}$, we can assume around 10 times greater. Then

$$\Rightarrow R_{eff} C_1 \approx 10 \times \frac{1}{\omega_1} \Rightarrow C_1 \approx \frac{10}{(801K)} \times \frac{1}{2\pi(1K)} \approx 1.986nF$$

c) Incremental transfer function is

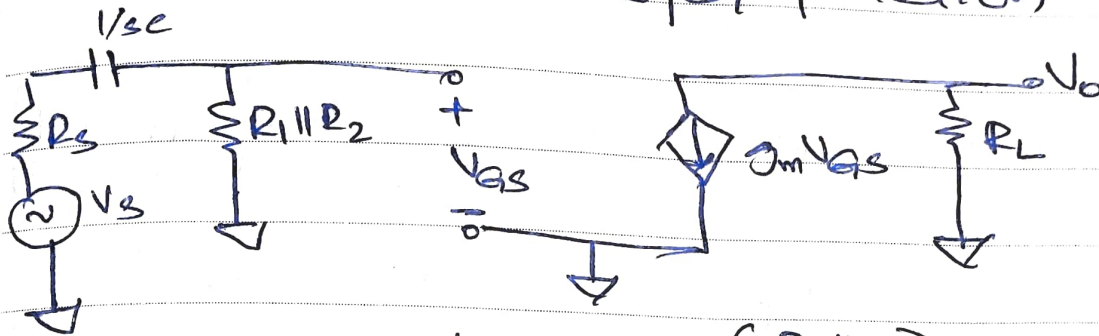

$$\Rightarrow V_{GS} = \frac{V_s (R_1 || R_2)}{R_s + \frac{1}{sC} + (R_1 || R_2)}$$

And $V_o = -g_m V_{GS} R_L$


$$\Rightarrow \frac{V_o(s)}{V_s(s)} = \frac{-g_m R_L (R_1 || R_2)}{R_s + (R_1 || R_2) + \frac{1}{sC}}$$

General T.F : $\frac{SCR}{1+SRC}$


Substituting values give

$$\Rightarrow \frac{V_o}{V_s} = \frac{15.84 \times 10^{-3} s}{1 + s (1.585 \times 10^{-3})}$$


$\frac{1}{630.914}$

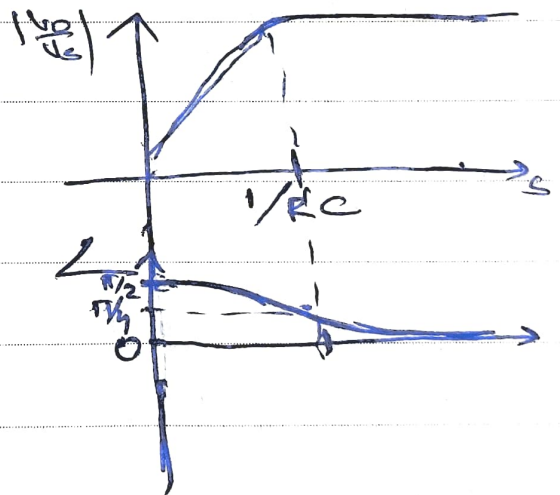

∴ Bode Plot :

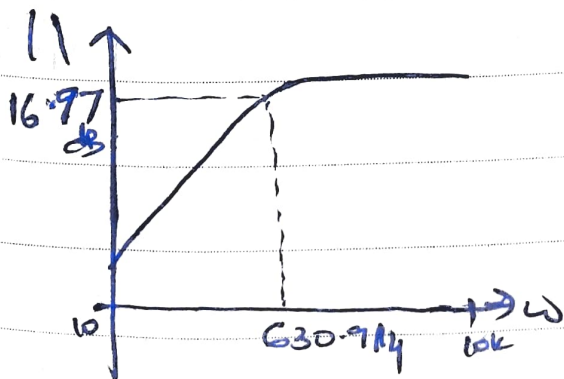

Magnitude

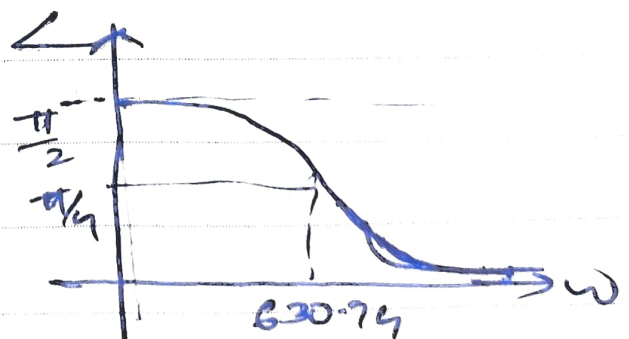

Phase